

Begin your response to **QUESTION 2** on this page.

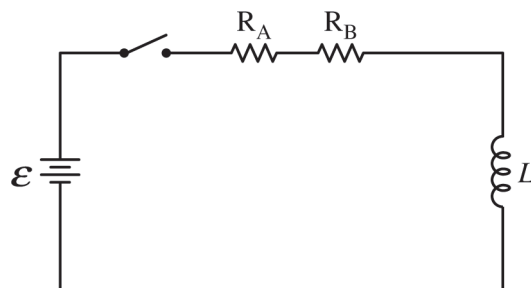


Figure 1

2. Students are asked to determine the resistance R of identical resistors R_A and R_B . The resistors are connected in series with each other, a battery of known emf \mathcal{E} , an inductor of known inductance L , and a switch, as shown in Figure 1. The students have access to a voltmeter that can measure potential difference as a function of time. The students are required to measure a quantity that increases with time to determine R .

(a)

- i. On the circuit diagram shown in Figure 1, **draw** the voltmeter, using the following symbol, with connections that would allow the students to correctly measure a potential difference that increases with time.



Voltmeter Symbol

- ii. **Describe** a procedure for collecting data that would allow the students to graphically determine the experimental value for R using a measured quantity that increases with time. Provide enough detail so that another student could replicate the experiment.

GO ON TO THE NEXT PAGE.

Continue your response to **QUESTION 2** on this page.

(b)

i. On the axes shown in Figure 2, produce a graph that represents the expected trend of the data by completing the following tasks.

- **Label** the quantities graphed on the vertical and horizontal axes.
- **Sketch** a line or curve that represents the expected trend of the collected data.
- **Label** any appropriate intercepts and/or asymptotes in terms of the quantities provided.



Figure 2

ii. **Describe** how the information from the graph in part (b)(i) would be used to determine the experimental value for R .

GO ON TO THE NEXT PAGE.

Continue your response to **QUESTION 2** on this page.

- (c) Starting with an appropriate application of Kirchhoff's loop rule, **derive**, but do NOT solve, a differential equation that can be used to determine the current I in the inductor at time t after the switch is closed. Express your answer in terms of R , \mathcal{E} , L , t , and physical constants, as appropriate.

After reaching steady state, the absolute value of the potential difference across R_A is $|\Delta V_1|$. The students replace the original inductor with a new inductor that has nonnegligible resistance. The experiment is repeated. After a long time, the absolute value of the potential difference across R_A is $|\Delta V_2|$.

- (d) **Indicate** whether $|\Delta V_2|$ is greater than, less than, or equal to $|\Delta V_1|$.

_____ $|\Delta V_2| > |\Delta V_1|$ _____ $|\Delta V_2| < |\Delta V_1|$ _____ $|\Delta V_2| = |\Delta V_1|$

Justify your answer.

GO ON TO THE NEXT PAGE.

Begin your response to **QUESTION 3** on this page.

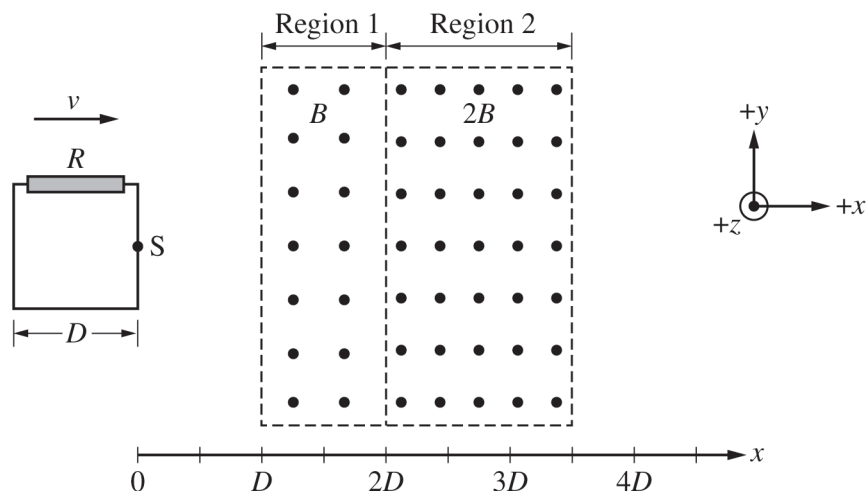



Figure 1

3. A wire is connected to a resistor of resistance R to form a rigid square loop of side length D . An external force is exerted on the loop so that the loop always moves with constant speed v in the $+x$ direction, as shown in Figure 1. The loop then enters Region 1 of external uniform magnetic field of magnitude B that is directed in the $+z$ -direction. Region 1 has boundaries $x = D$ and $x = 2D$. The loop later enters Region 2 of external uniform magnetic field of magnitude $2B$ that is directed in the $+z$ -direction. Region 2 has boundaries $x = 2D$ and $x = 3.5D$. Point S is the midpoint of the leading edge of the loop.

GO ON TO THE NEXT PAGE.

Question 2: Free-Response Question**15 points**

- (a)(i)** For correctly placing the voltmeter in parallel with Resistor A , Resistor B , or the combination of resistors A and B **1 point**

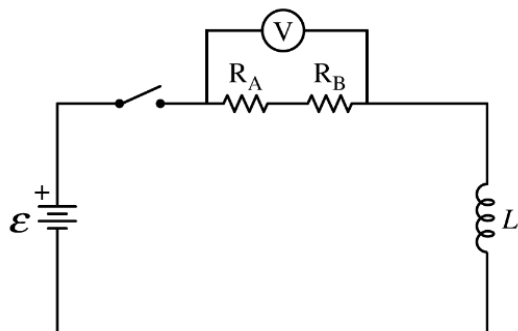Example Response

- (a)(ii)** For a procedure that indicates that the voltmeter should be used to measure the potential difference for at least one time **1 point**



For measuring the potential difference from immediately after the switch is closed to when steady-state conditions have been established or until a time at which the time constant can be determined **1 point**

Example Response

Close the switch. Using the voltmeter, record the potential difference as a function of time until steady-state conditions are established.

Total for part (a) 3 points

- (b)(i)** For correctly labeling potential difference on the vertical axis and time on the horizontal axis **1 point**
- For a concave-down and increasing curve **1 point**
- For a curve that starts at the origin and asymptotically approaches a nonzero potential difference value **1 point**
- For correctly labeling the horizontal asymptote that is consistent with the indication of the connection of the voltmeter in the response in part (a)(i) **1 point**

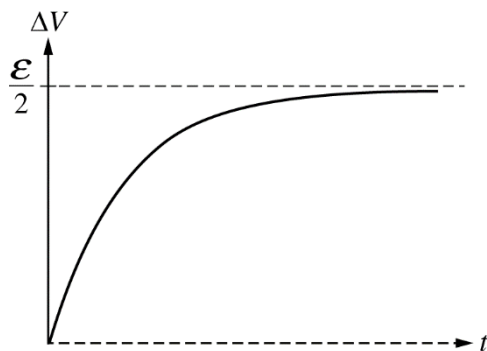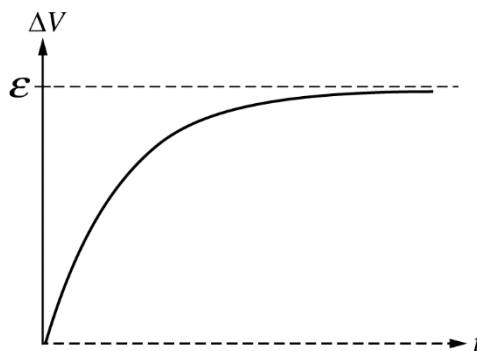Example Responses*One Resistor**Combination of Resistors***OR**

(b)(ii) For indicating that a curve fit to the graph is that of an exponential function **1 point**

Alternate Solution

For indicating the time on the graph where the potential difference across Resistor A or Resistor B is approximately $\frac{0.63\mathcal{E}}{2}$ or that the potential difference across the combination of resistors A and B is approximately $0.63\mathcal{E}$

For indicating that the coefficient in front of the t of the curve-fit equation is equal to $\frac{2R}{L}$ **1 point**

Alternate Solution

For indicating that the time constant is equal to $\frac{L}{2R}$

Example Response

The data in the graph should be fit with an exponential function for the equation

$$V_R = \mathcal{E} \left(1 - e^{-t \frac{2R}{L}} \right). \text{ Because } \mathcal{E} \text{ and } L \text{ are known, } R \text{ can be calculated.}$$

Alternate Example Response

The potential difference at $0.63\mathcal{E}$ along the vertical axis corresponds to the time constant along the horizontal axis. Because the time constant is equal to $\frac{L}{2R}$, and L is known, R can be calculated.

Total for part (b) 6 points