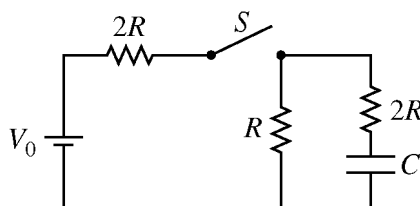


**2019 AP<sup>®</sup> PHYSICS C: ELECTRICITY AND MAGNETISM FREE-RESPONSE QUESTIONS****PHYSICS C: ELECTRICITY AND MAGNETISM****SECTION II****Time—45 minutes****3 Questions**

**Directions:** Answer all three questions. The suggested time is about 15 minutes for answering each of the questions, which are worth 15 points each. The parts within a question may not have equal weight. Show all your work in this booklet in the spaces provided after each part.



1. The circuit represented above is composed of three resistors with the resistances shown, a battery of voltage  $V_0$ , a capacitor of capacitance  $C$ , and a switch  $S$ . The switch is closed, and after a long time, the circuit reaches steady-state conditions. Answer the following questions in terms of  $V_0$ ,  $R$ ,  $C$ , and fundamental constants, as appropriate.
- (a) Derive an expression for the steady-state current supplied by the battery.
  - (b) Derive an expression for the charge on the capacitor.
  - (c) Derive an expression for the energy stored in the capacitor.
- Now the switch is opened at time  $t = 0$ .
- (d) Write, but do NOT solve, a differential equation that could be used to solve for the charge  $q(t)$  on the capacitor as a function of the time  $t$  after the switch is opened.

## 2019 AP<sup>®</sup> PHYSICS C: ELECTRICITY AND MAGNETISM FREE-RESPONSE QUESTIONS

(e)

- i. Calculate the current in resistor R immediately after the switch is opened.
- ii. On the axes below, sketch the current in the circuit as a function of time from time  $t = 0$  to a long time after the switch is opened. Explicitly label the maxima with numerical values or algebraic expressions, as appropriate.




- (f) Is the total amount of energy dissipated in the resistors after the switch is opened greater than, less than, or equal to the amount of energy stored in the capacitor calculated in part (c) ?

\_\_\_\_ Greater than      \_\_\_\_ Less than      \_\_\_\_ Equal to

Justify your answer.
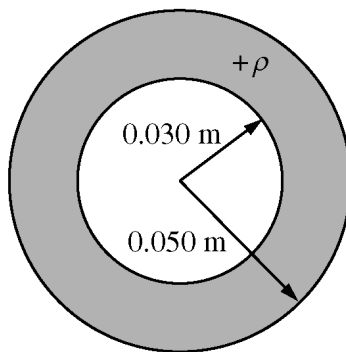
# 2019 AP<sup>®</sup> PHYSICS C: ELECTRICITY AND MAGNETISM FREE-RESPONSE QUESTIONS




2. A nonconducting hollow sphere of inner radius 0.030 m and outer radius 0.050 m carries a positive volume charge density  $\rho$ , as shown in the figure above. The charge density  $\rho$  of the sphere is given as a function of the distance  $r$  from the center of the sphere, in meters, by the following.

$$r < 0.030 \text{ m: } \rho = 0$$

$$0.030 \text{ m} < r < 0.050 \text{ m: } \rho = b/r, \text{ where } b = 1.6 \times 10^{-6} \text{ C/m}^2$$

$$r > 0.050 \text{ m: } \rho = 0$$

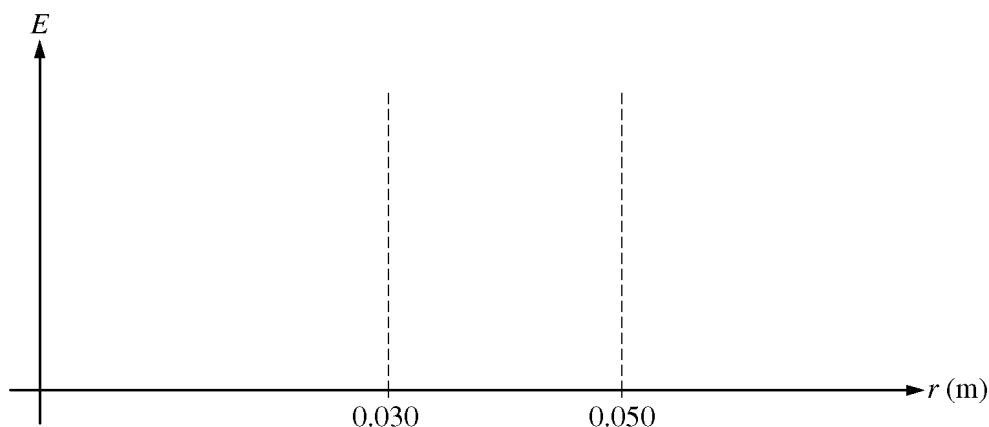- Calculate the total charge of the sphere.
- Using Gauss's law, calculate the magnitude of the electric field  $E$  at the outer surface of the sphere.
- On the axes below, sketch the magnitude of the electric field  $E$  as a function of distance  $r$  from the center of the sphere.




# AP<sup>®</sup> PHYSICS C: ELECTRICITY AND MAGNETISM

## 2019 SCORING GUIDELINES

### Question 1

**15 points**

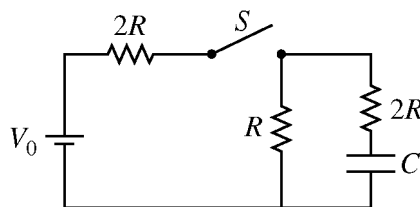

The circuit represented above is composed of three resistors with the resistances shown, a battery of voltage  $V_0$ , a capacitor of capacitance  $C$ , and a switch  $S$ . The switch is closed, and after a long time, the circuit reaches steady-state conditions. Answer the following questions in terms of  $V_0$ ,  $R$ ,  $C$ , and fundamental constants, as appropriate.

- (a) LO CNV-7.B.a, SP 5.A, 5.E  
2 points

Derive an expression for the steady-state current supplied by the battery.

For using Ohm's law		1 point
$I = \frac{V}{R_{eff}} = \frac{V_0}{(2R + R)}$		
For correct substitution leading to correct answer		1 point
$I = \frac{V_0}{3R}$		

- (b) LO CNV-7.B.b, SP 5.A, 5.E  
2 points

Derive an expression for the charge on the capacitor.

For using the equation relating stored charge to capacitance		1 point
$q = CV = CV_C = CV_R$		
For determining $V_R$ and substituting into the above equation		1 point
$V_R = IR = \left( \frac{V_0}{3R} \right) R = \frac{1}{3} V_0$		
$q = CV_R = C \left( \frac{1}{3} V_0 \right) = \frac{1}{3} CV_0$		

# AP<sup>®</sup> PHYSICS C: ELECTRICITY AND MAGNETISM

## 2019 SCORING GUIDELINES

### Question 1 (continued)

- (c) LO CNV-7.B.b, SP 5.A, 5.E  
2 points

Derive an expression for the energy stored in the capacitor.

For any correct equation for energy stored in a capacitor		1 point
$U = \frac{q^2}{2C}$		
Substitute charge and/or voltage from part (b)		1 point
$U = \frac{(CV_0/3)^2}{2C} = \frac{1}{18} CV_0^2$		

Now the switch is opened at time  $t = 0$ .

- (d) LO CNV-7.D.a, SP 5.A, 5.E  
2 points

Write, but do NOT solve, a differential equation that could be used to solve for the charge  $q(t)$  on the capacitor as a function of the time  $t$  after the switch is opened.

For any correct voltage loop equation		1 point
$V_C - V_R - V_{2R} = 0 \therefore V_C = V_R + V_{2R}$		
$\frac{q(t)}{C} = I(R + 2R)$		
<u>Note:</u> Any correct loop equation for when the switch is open earns the point		
For substituting $-dq/dt$ or $dq/dt$ for the current, consistent with loop equation		1 point
$\frac{q(t)}{C} = -3R \frac{dq}{dt}$		

# **AP<sup>®</sup> PHYSICS C: ELECTRICITY AND MAGNETISM**

## **2019 SCORING GUIDELINES**

### **Question 1 (continued)**

#### **Learning Objectives**

**CNV-7.B.a:** Calculate the potential difference across a capacitor in a circuit arrangement containing capacitors, resistors, and an energy source under steady-state conditions.

**CNV-7.B.b:** Calculate the stored charge on a capacitor in a circuit arrangement containing capacitors, resistors, and an energy source under steady-state conditions.

**CNV-7.D.a:** Derive expressions using calculus to describe the time dependence of the stored charge or potential difference across the capacitor, or the current or potential difference across the resistor in an RC circuit when charging or discharging a capacitor.

**CNV-7.E.b:** Describe the behavior of the voltage or current behavior over time for a circuit that contains resistors and capacitors in a multi-loop arrangement.

**CNV-7.G.a:** Describe the energy transfer in charging or discharging a capacitor in an RC circuit.

#### **Science Practices**

**3.C:** Sketch a graph that shows a functional relationship between two quantities.

**5.A:** Select an appropriate law, definition, or mathematical relationship or model to describe a physical situation.

**5.E:** Derive a symbolic expression from known quantities by selecting and following a logical algebraic pathway.

**7.A:** Make a scientific claim.

**7.C:** Support a claim with evidence from physical representations.