

2000 AP<sup>®</sup> PHYSICS C FREE-RESPONSE QUESTIONS


PHYSICS C

Section II, ELECTRICITY AND MAGNETISM

Time—45 minutes

3 Questions

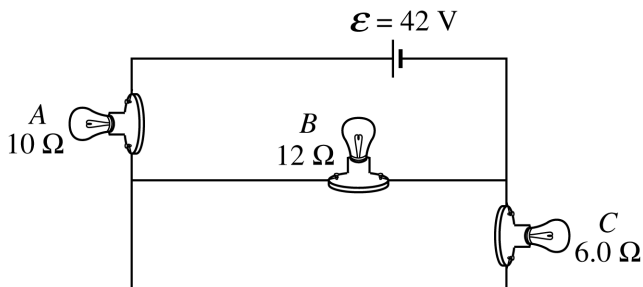
**Directions:** Answer all three questions. The suggested time is about 15 minutes for answering each of the questions, which are worth 15 points each. The parts within a question may not have equal weight. Show all your work in the pink booklet in the spaces provided after each part, NOT in this green insert.



E & M 1.

Lightbulbs  $A$ ,  $B$ , and  $C$  are connected in the circuit shown above.

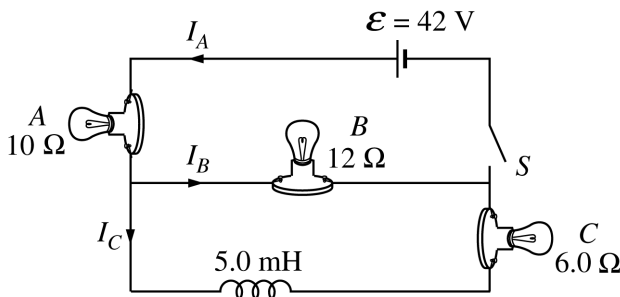- (a) List the bulbs in order of their brightness, from brightest to least bright. If any bulbs have the same brightness, state which ones. Justify your answer.




Now a switch  $S$  and a 5.0 mH inductor are added to the circuit, as shown above. The switch is closed at time  $t = 0$ .

- (b) Determine the currents  $I_A$ ,  $I_B$ , and  $I_C$  for the following times.
- Immediately after the switch is closed
  - A long time after the switch is closed

2000 AP® PHYSICS C FREE-RESPONSE QUESTIONS

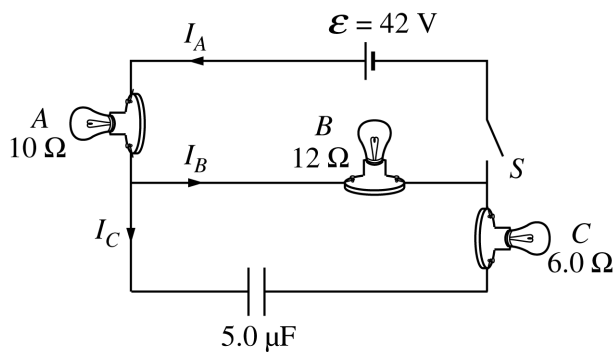- (c) On the axes below, sketch the magnitude of the potential difference  $V_L$  across the inductor as a function of time, from immediately after the switch is closed until a long time after the switch is closed.



- (d) Now consider a similar circuit with an uncharged  $5.0\ \mu\text{F}$  capacitor instead of the inductor, as shown above. The switch is again closed at time  $t = 0$ . On the axes below, sketch the magnitude of the potential difference  $V_{\text{cap}}$  across the capacitor as a function of time, from immediately after the switch is closed until a long time after the switch is closed.



2000 AP® PHYSICS C FREE-RESPONSE QUESTIONS

E & M 2.

Three particles,  $A$ ,  $B$ , and  $C$ , have equal positive charges  $Q$  and are held in place at the vertices of an equilateral triangle with sides of length  $\ell$ , as shown in the figures below. The dotted lines represent the bisectors for each side. The base of the triangle lies on the  $x$ -axis, and the altitude of the triangle lies on the  $y$ -axis.

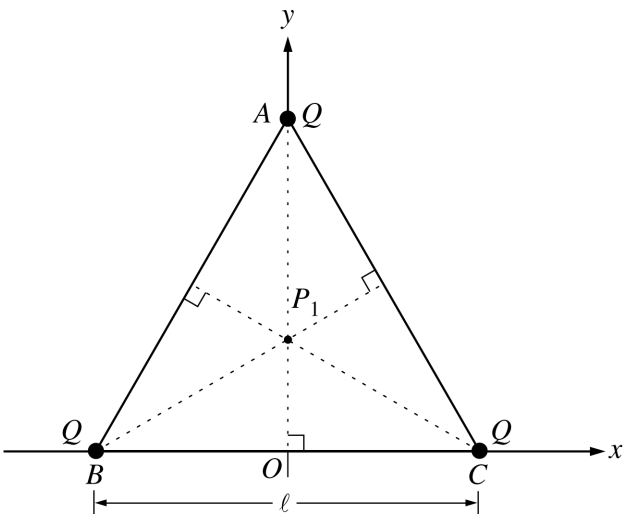


Figure 1

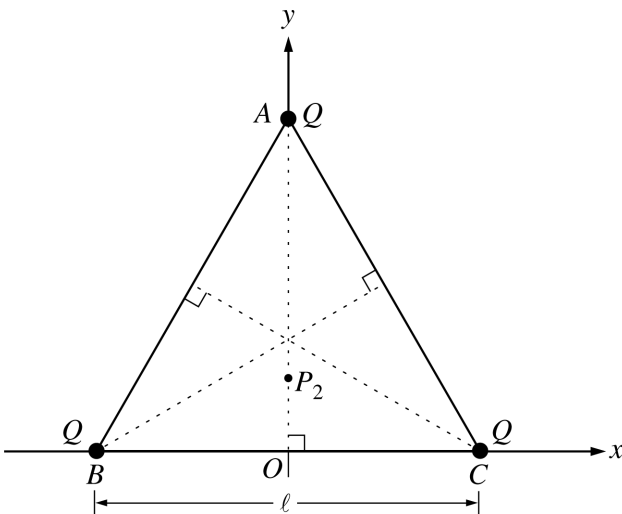


Figure 2

(a)

- i. Point  $P_1$ , the intersection of the three bisectors, locates the geometric center of the triangle and is one point where the electric field is zero. On Figure 1 above, draw the electric field vectors  $\mathbf{E}_A$ ,  $\mathbf{E}_B$ , and  $\mathbf{E}_C$  at  $P_1$  due to each of the three charges. Be sure your arrows are drawn to reflect the relative magnitude of the fields.
- ii. Another point where the electric field is zero is point  $P_2$  at  $(0, y_2)$ . On Figure 2 above, draw electric field vectors  $\mathbf{E}_A$ ,  $\mathbf{E}_B$ , and  $\mathbf{E}_C$  at  $P_2$  due to each of the three point charges. Indicate below whether the magnitude of each of these vectors is greater than, less than, or the same as for point  $P_1$ .

	Greater than at $P_1$	Less than at $P_1$	The same as at $P_1$
$E_A$			
$E_B$			
$E_C$			

E&amp;M. 1 (15 points)

(a) 4 points

Since brightness is proportional to the power dissipated by a bulb, the answer may be found by solving the circuit to determine the power dissipated by each bulb. For example,

$$\frac{1}{R_p} = \frac{1}{12\ \Omega} + \frac{1}{6\ \Omega} = \frac{3}{12\ \Omega}, \text{ where } R_p \text{ is the resistance of the parallel combination of resistors}$$

$$R_p = 4\ \Omega$$

$$I_A = \frac{\mathcal{E}}{R_A + R_p} = \frac{42\ \text{V}}{10\ \Omega + 4\ \Omega} = 3\ \text{A}$$

$$I_B = \frac{V_p}{R_B} = \frac{I_A R_p}{R_B} = \frac{(3\ \text{A})(4\ \Omega)}{12\ \Omega} = 1\ \text{A}$$

$$I_C = \frac{V_p}{R_C} = \frac{I_A R_p}{R_C} = \frac{3 \cdot 4(3\ \text{A})(4\ \Omega)}{6\ \Omega} = 2\ \text{A}$$

$$P_A = I_A^2 R_A = (3\ \text{A})^2 (10\ \Omega) = 90\ \text{W}$$

$$P_B = I_B^2 R_B = (1\ \text{A})^2 (12\ \Omega) = 12\ \text{W}$$

$$P_C = I_C^2 R_C = (2\ \text{A})^2 (6\ \Omega) = 24\ \text{W}$$

For correct ordering, i.e., bulb *A* is brighter than bulb *C*, which is brighter than bulb *B* (Partial credit of 1 point given for incorrect answer but with an indication that bulb *A* is brightest or that bulb *C* is brighter than bulb *B*.)

For a correct explanation, which can be by a quantitative solution for the currents and powers as above, or by a qualitative approach that notes that all the current in the circuit flows through bulb *A*, then branches in such a way that bulb *C* receives more current than bulb *B*.

3 points

1 point

(b)

i. 3 points

Immediately after the switch is closed there is no current in the inductor so the circuit consists of resistors *A* and *B* in series with the source of emf.

For  $I_C = 0$

For recognition that  $I_A = I_B$  and they are nonzero

For correct numerical answers for  $I_A$  and  $I_B$ , i.e.,  $I_A = I_B = \frac{42\ \text{V}}{10\ \Omega + 12\ \Omega} = 1.91\ \text{A}$

1 point

1 point

1 point