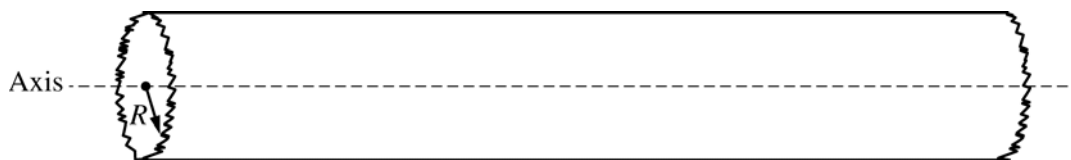


2013 AP[®] PHYSICS C: ELECTRICITY AND MAGNETISM FREE-RESPONSE QUESTIONS**PHYSICS C: ELECTRICITY AND MAGNETISM****SECTION II****Time—45 minutes****3 Questions**

Directions: Answer all three questions. The suggested time is about 15 minutes for answering each of the questions, which are worth 15 points each. The parts within a question may not have equal weight. Show all your work in this booklet in the spaces provided after each part.




E&M 1.

A very long, solid, nonconducting cylinder of radius R has a positive charge of uniform volume density ρ .

A section of the cylinder far from its ends is shown in the diagram above. Let r represent the radial distance from the axis of the cylinder. Express all answers in terms of r , R , ρ , and fundamental constants, as appropriate.

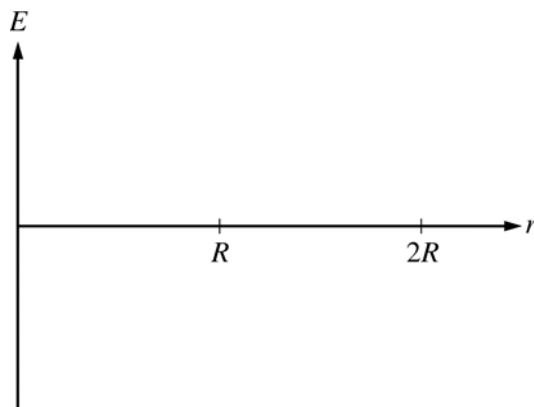
- (a) Using Gauss's law, derive an expression for the magnitude of the electric field at a radius $r < R$. Draw an appropriate Gaussian surface on the diagram.
- (b) Using Gauss's law, derive an expression for the magnitude of the electric field at a radius $r > R$.
- (c) On the axes below, sketch the graph of electric field E as a function of radial distance r for $r = 0$ to $r = 2R$. Explicitly label any intercepts, asymptotes, maxima, or minima with numerical values or algebraic expressions, as appropriate.




- (d)
 - i. Derive an expression for the magnitude of the potential difference between $r = 0$ and $r = R$.
 - ii. Is the potential higher at $r = 0$ or $r = R$?
_____ $r = 0$ _____ $r = R$

2013 AP[®] PHYSICS C: ELECTRICITY AND MAGNETISM FREE-RESPONSE QUESTIONS

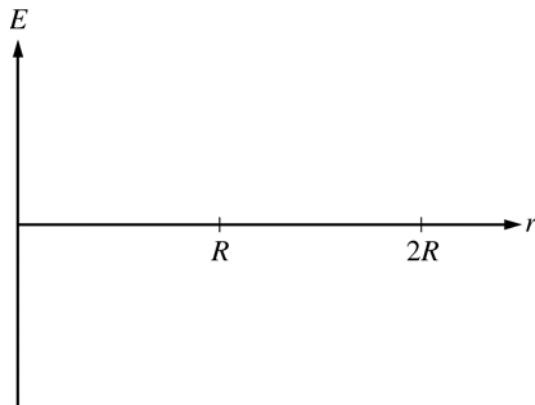- (e) The nonconducting cylinder is replaced with a conducting cylinder of the same shape and same linear charge density. On the axes below, sketch the electric field E as a function of r for $r = 0$ to $r = 2R$. Explicitly label any intercepts, asymptotes, maxima, or minima with numerical values or algebraic expressions, as appropriate.



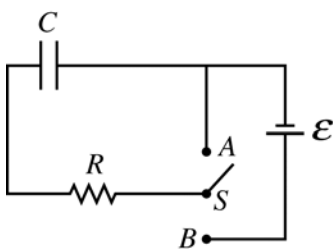2013 AP[®] PHYSICS C: ELECTRICITY AND MAGNETISM FREE-RESPONSE QUESTIONS



E&M 2.

In a lab, you set up a circuit that contains a capacitor C , a resistor R , a switch S , and a power supply, as shown in the diagram above. The capacitor is initially uncharged. The switch, which is initially open, can be moved to positions A or B .

(a)

- i. Indicate the position to which the switch should be moved to charge the capacitor.

___ A ___ B

- ii. On the diagram, draw a voltmeter that is properly connected to the circuit in a manner that will allow the voltage to be measured across the capacitor.

After a long time you move the switch to discharge the capacitor, and your lab partner starts a stopwatch. You collect the following measurements of the voltage across the capacitor at various times.

t (s)	6	18	30	42	54
V (V)	252	74	33	10	6

You wish to determine the time constant τ of the circuit from the slope of a linear graph.

(b)

- i. Indicate two quantities you would plot to obtain a linear graph.
- ii. Use the remaining rows in the table above, as needed, to record any quantities that you indicated that are not given. Label each row you use and include units.