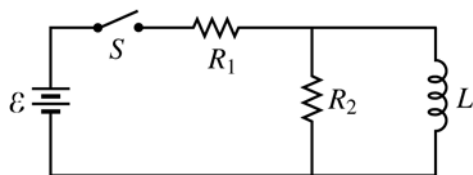


**2005 AP<sup>®</sup> PHYSICS C: ELECTRICITY AND MAGNETISM**  
**FREE-RESPONSE QUESTIONS**



E&M. 2.

In the circuit shown above, resistors 1 and 2 of resistance  $R_1$  and  $R_2$ , respectively, and an inductor of inductance  $L$  are connected to a battery of emf  $\mathcal{E}$  and a switch  $S$ . The switch is closed at time  $t = 0$ . Express all algebraic answers in terms of the given quantities and fundamental constants.


- (a) Determine the current through resistor 1 immediately after the switch is closed.
- (b) Determine the magnitude of the initial rate of change of current,  $dI/dt$ , in the inductor.
- (c) Determine the current through the battery a long time after the switch has been closed.
- (d) On the axes below, sketch a graph of the current through the battery as a function of time.



Some time after steady state has been reached, the switch is opened.

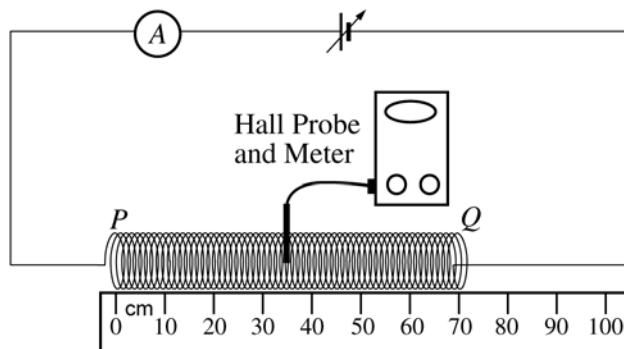- (e) Determine the voltage across resistor 2 just after the switch has been opened.

**2005 AP<sup>®</sup> PHYSICS C: ELECTRICITY AND MAGNETISM  
FREE-RESPONSE QUESTIONS**



E&M. 3.

A student performs an experiment to measure the magnetic field along the axis of the long, 100-turn solenoid *PQ* shown above. She connects ends *P* and *Q* of the solenoid to a variable power supply and an ammeter as shown. End *P* of the solenoid is taped at the 0 cm mark of a meterstick. The solenoid can be stretched so that the position of end *Q* can be varied. The student then positions a Hall probe\* in the center of the solenoid to measure the magnetic field along its axis. She measures the field for a fixed current of 3.0 A and various positions of the end *Q*. The data she obtains are shown below.

Trial	Position of End <i>Q</i> (cm)	Measured Magnetic Field (T) (directed from <i>P</i> to <i>Q</i> )	<i>n</i> (turns/m)
1	40	$9.70 \times 10^{-4}$	
2	50	$7.70 \times 10^{-4}$	
3	60	$6.80 \times 10^{-4}$	
4	80	$4.90 \times 10^{-4}$	
5	100	$4.00 \times 10^{-4}$	

(a) Complete the last column of the table above by calculating the number of turns per meter.

\*A Hall Probe is a device used to measure the magnetic field at a point.

**AP<sup>®</sup> PHYSICS C ELECTRICITY & MAGNETISM  
2005 SCORING GUIDELINES**

**Question 2 (continued)**

**Distribution  
of points**

(c) 2 points

After a long time the current is constant, so  $V_L = 0$ .

$V_L = V_{R_2} = 0$ , so a constant current goes through resistor 1 and the inductor.

$$V_{\text{batt}} = V_{R_1}$$

For the correct substitution of both voltage and resistance, using Ohm's law for  $V_{R_1}$

1 point


$$\mathcal{E} = I_{\text{batt}} R_1$$

For the correct answer

1 point

$$I_{\text{batt}} = \mathcal{E}/R_1$$

(d) 4 points

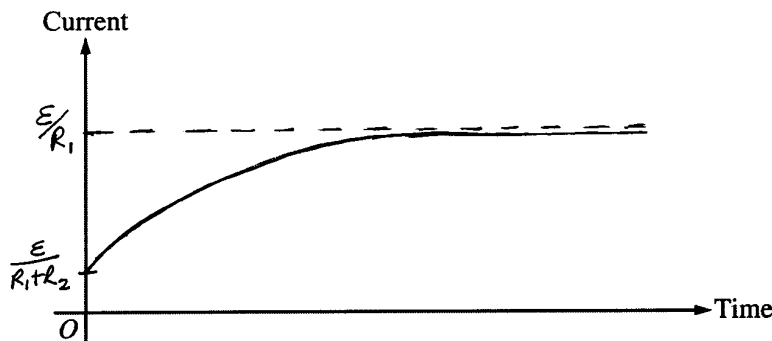

For a graph that rises asymptotically

1 point

This point must be earned in order to obtain any of the following points.

For starting the line above zero

1 point

For starting the line at the lower limit determined in (a)

1 point

For approaching the upper limit determined in part (c)

1 point

(e) 3 points

The current calculated in part (c) that was going through the inductor now goes through only resistor 2.

For correct application of the loop theorem

1 point

$$I_{R_2} = I_L, \text{ where } I_L \text{ equals } I_{\text{batt}} \text{ determined in (c)}$$

For correct substitution of both currents, using Ohm's law for  $I_{R_2}$  with a resistance  $R_2$

1 point

$$V_{R_2}/R_2 = \mathcal{E}/R_1$$

For a correct final answer

1 point

$$V_{R_2} = \mathcal{E}R_2/R_1$$