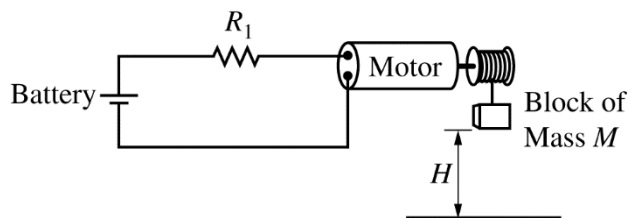


2019 AP[®] PHYSICS 1 FREE-RESPONSE QUESTIONS



4. (7 points, suggested time 13 minutes)

A motor is a device that when connected to a battery converts electrical energy into mechanical energy. The motor shown above is used to lift a block of mass M at constant speed from the ground to a height H above the ground in a time interval Δt . The motor has constant resistance and is connected in series with a resistor of resistance R_1 and a battery.

Mechanical power, the rate at which mechanical work is done on the block, increases if the potential difference (voltage drop) between the two terminals of the motor increases.

(a) Determine an expression for the mechanical power in terms of M , H , Δt , and physical constants, as appropriate.

(b) Without M or H being changed, the time interval Δt can be decreased by adding one resistor of resistance R_2 , where $R_2 > R_1$, to the circuit shown above. How should the resistor of resistance R_2 be added to the circuit to decrease Δt ?

☐ In parallel with the battery
 ☐ In parallel with R_1
 ☐ In parallel with the motor
 ☐ In series with the battery, R_1 , and the motor


In a clear, coherent, paragraph-length response that may also contain figures and/or equations, justify why your selection would decrease Δt .

AP[®] PHYSICS 1

2019 SCORING GUIDELINES

Question 4

7 points

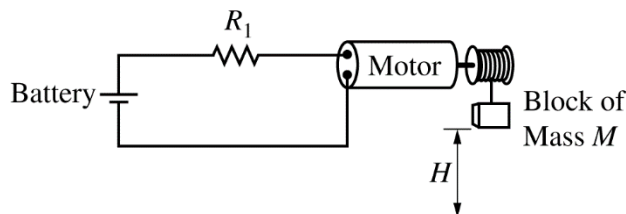

A motor is a device that when connected to a battery converts electrical energy into mechanical energy. The motor shown above is used to lift a block of mass M at constant speed from the ground to a height H above the ground in a time interval Δt . The motor has constant resistance and is connected in series with a resistor of resistance R_1 and a battery.

Mechanical power, the rate at which mechanical work is done on the block, increases if the potential difference (voltage drop) between the two terminals of the motor increases.

- (a) LO 5.B.5.5, SP 2.2
2 points

Determine an expression for the mechanical power in terms of M , H , Δt , and physical constants, as appropriate.

| | | |
|---|--|---------|
| For an expression that implies reasoning in terms of energy (as opposed to e.g., kinematics) | | 1 point |
| Example: MgH | | |
| For a correct expression for the power generated by the motor lifting the block at constant speed | | 1 point |
| $MgH/\Delta t$ | | |

- (b) LO 5.B.9.2, SP 4.2, 6.4, 7.2; LO 5.B.9.3, SP 6.4, 7.2
5 points

Without M or H being changed, the time interval Δt can be decreased by adding one resistor of resistance R_2 , where $R_2 > R_1$, to the circuit shown above. How should the resistor of resistance R_2 be added to the circuit to decrease Δt ?

☐ In parallel with the battery
 ☐ In parallel with R_1
 ☐ In parallel with the motor
 ☐ In series with the battery, R_1 , and the motor

In a clear, coherent, paragraph-length response that may also contain figures and/or equations, justify why your selection would decrease Δt .

| | | |
|---|--|--|
| Correct answer: "In parallel with R_1 " | | |
| <u>Note:</u> If the wrong selection is made, the justification may still earn credit. | | |

AP[®] PHYSICS 1

2019 SCORING GUIDELINES

Question 4 (continued)

(b) (continued)

| | | |
|--|--|---------|
| For a justification that correctly asserts that power must increase for Δt to decrease, or correctly asserting that the faster the rate of energy transfer means that work gets done in a smaller time interval | | 1 point |
| For a correct assertion that current increases as resistance of the circuit decreases <i>Alternate Method: Potential difference across the parallel resistors will decrease if their resistance decreases.</i> | | 1 point |
| For making the connection that there is an increase in current specifically in the motor because it is the same as the total current in the circuit <i>Alternate Method: There is an increase in potential difference specifically across the motor because the potential difference across the parallel resistors decreases (Kirchhoff's loop rule).</i> | | 1 point |
| For a justification that indicates that connecting R_2 in parallel with R_1 will decrease the equivalent resistance of the circuit | | 1 point |
| For a logical, relevant, and internally consistent argument that addresses the required argument or question asked, and follows the guidelines described in the published requirements for the paragraph-length response | | 1 point |

| | | |
|--|--|--|
| <p>Example Paragraph Response 1:</p> <p>The work required to lift the block is MgH, so the rate at which the motor must do work to lift the block in the given time is $W/\Delta t = MgH/\Delta t$. The rate at which the motor does work increases with the potential difference across the motor (<u>Note</u>: This information is given in the question, so no points allotted in rubric for this statement.) To decrease the time, the motor must increase the rate at which the work is done, which requires a larger potential difference across the motor (or a larger current through the motor because $\Delta V = IR$). To increase the potential difference across the motor, the potential difference across R_1 must decrease, by Kirchhoff's loop rule (for a loop containing the battery, the motor and R_1). When R_2 is placed in parallel with R_1 the equivalent resistance of the combination decreases and the potential difference across that section decreases.</p> | | |
| <p>Example Paragraph Response 2:</p> <p>Resistor R_2 should be connected in parallel with R_1. This will result in a smaller equivalent resistance in series with the battery and motor, so the current in the circuit (and through the motor) will be larger. The larger motor current results in the motor having a higher mechanical power. Because this power $MgH/\Delta t$ is larger and MgH is constant, the time interval Δt will be smaller.</p> | | |

AP[®] PHYSICS 1
2019 SCORING GUIDELINES

Question 4 (continued)

Learning Objectives

- LO 5.B.5.5:** The student is able to predict and calculate the energy transfer to (i.e., the work done on) an object or system from information about a force exerted on the object or system through a distance. [See Science Practices 2.2, 6.4]
- LO 5.B.9.2:** The student is able to apply conservation of energy concepts to the design of an experiment that will demonstrate the validity of Kirchhoff's loop rule ($\Sigma\Delta V = 0$) in a circuit with only a battery and resistors either in series or in, at most, one pair of parallel branches. [See Science Practices 4.2, 6.4, 7.2]
- LO 5.B.9.3:** The student is able to apply conservation of energy (Kirchhoff's loop rule) in calculations involving the total electric potential difference for complete circuit loops with only a single battery and resistors in series and/or in, at most, one parallel branch. [See Science Practices 2.2, 6.4, 7.2]