

## PHYSICS C: ELECTRICITY AND MAGNETISM

## SECTION II

Time—45 minutes

3 Questions

**Directions:** Answer all three questions. The suggested time is about 15 minutes for answering each of the questions, which are worth 15 points each. The parts within a question may not have equal weight. Show all your work in the pink booklet in the spaces provided after each part, NOT in this green insert.

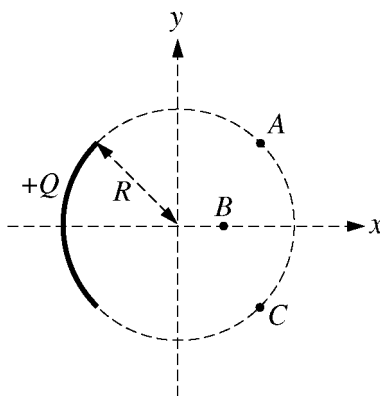


Figure I

E&amp;M. 1.

A charge  $+Q$  is uniformly distributed over a quarter circle of radius  $R$ , as shown above. Points  $A$ ,  $B$ , and  $C$  are located as shown, with  $A$  and  $C$  located symmetrically relative to the  $x$ -axis. Express all algebraic answers in terms of the given quantities and fundamental constants.

- (a) Rank the magnitude of the electric potential at points  $A$ ,  $B$ , and  $C$  from greatest to least, with number 1 being greatest. If two points have the same potential, give them the same ranking.

\_\_\_\_\_  $V_A$       \_\_\_\_\_  $V_B$       \_\_\_\_\_  $V_C$

Justify your rankings.

Point  $P$  is at the origin, as shown below, and is the center of curvature of the charge distribution.


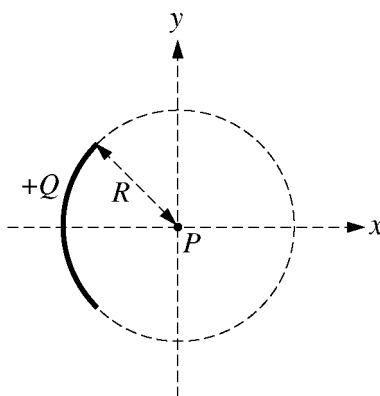



Figure II

**2010 AP<sup>®</sup> PHYSICS C: ELECTRICITY AND MAGNETISM FREE-RESPONSE QUESTIONS**

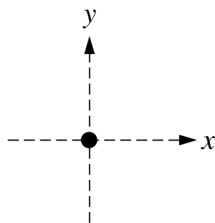- (b) Determine an expression for the electric potential at point  $P$  due to the charge  $Q$ .
- (c) A positive point charge  $q$  with mass  $m$  is placed at point  $P$  and released from rest. Derive an expression for the speed of the point charge when it is very far from the origin.
- (d) On the dot representing point  $P$  below, indicate the direction of the electric field at point  $P$  due to the charge  $Q$ .



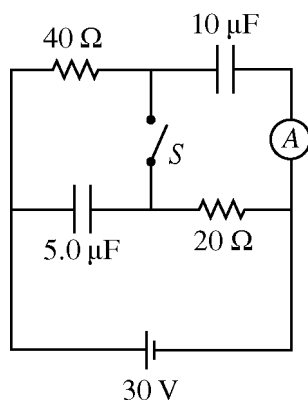- (e) Derive an expression for the magnitude of the electric field at point  $P$ .



E&M. 2.

In the circuit illustrated above, switch  $S$  is initially open and the battery has been connected for a long time.

- (a) What is the steady-state current through the ammeter?
- (b) Calculate the charge on the  $10\ \mu\text{F}$  capacitor.
- (c) Calculate the energy stored in the  $5.0\ \mu\text{F}$  capacitor.

The switch is now closed, and the circuit comes to a new steady state.

- (d) Calculate the steady-state current through the battery.
- (e) Calculate the final charge on the  $5.0\ \mu\text{F}$  capacitor.
- (f) Calculate the energy dissipated as heat in the  $40\ \Omega$  resistor in one minute once the circuit has reached steady state.